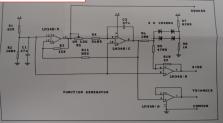




Close-up of the schematic

If you can't read a schematic, don't worry. I will give a close-up picture of the completed circuit layout.




	COMPONENTS	
Resistor	s, 5%, 1/4W	
560R	green blue brown	1
820R	grey red brown	i
1K	brown black red	i
8K2	grey red red	1
10K	brown black orange	1
15K	brown green orange	1
82K	grey red orange	1
100K	brown black yellow	1
470K	yellow violet yellow	1
1M	brown black green	,
1M Piher	log pot + spindle	,
1N4004 d	liode	1
9V battery snap		
47nF ceramic capacitor		1
LM348 IC	time capacitor	2
4 pin IC		1
Kit 23 pcb	SOCKEL	1

Pictured Here:

This is the value sheet that comes with the kit23 F6. You'll notice that the values are all layed out so you can easily pick out the correct value compnent and match it to the proper location on the PCB. We replace 3 stock items with R5 replacements. We use a LM324

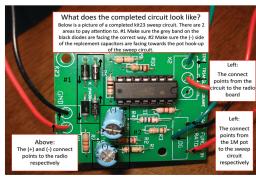We use a LM324 in place of the LM348 op amp. We use RS (272-1027) caps in place of the stock caps and a 1M linear taper pot (271-0211) in place of the plastic 1M pot spplied.





Left:

board Left:

circuit

